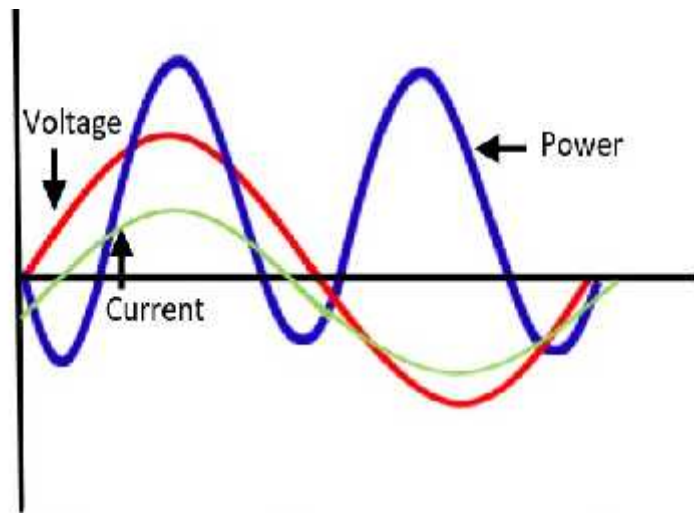



# Power in AC circuits


# Power factor




Plot of the Power of Instantaneous Voltage,  
Current & Power

Circuit Globe

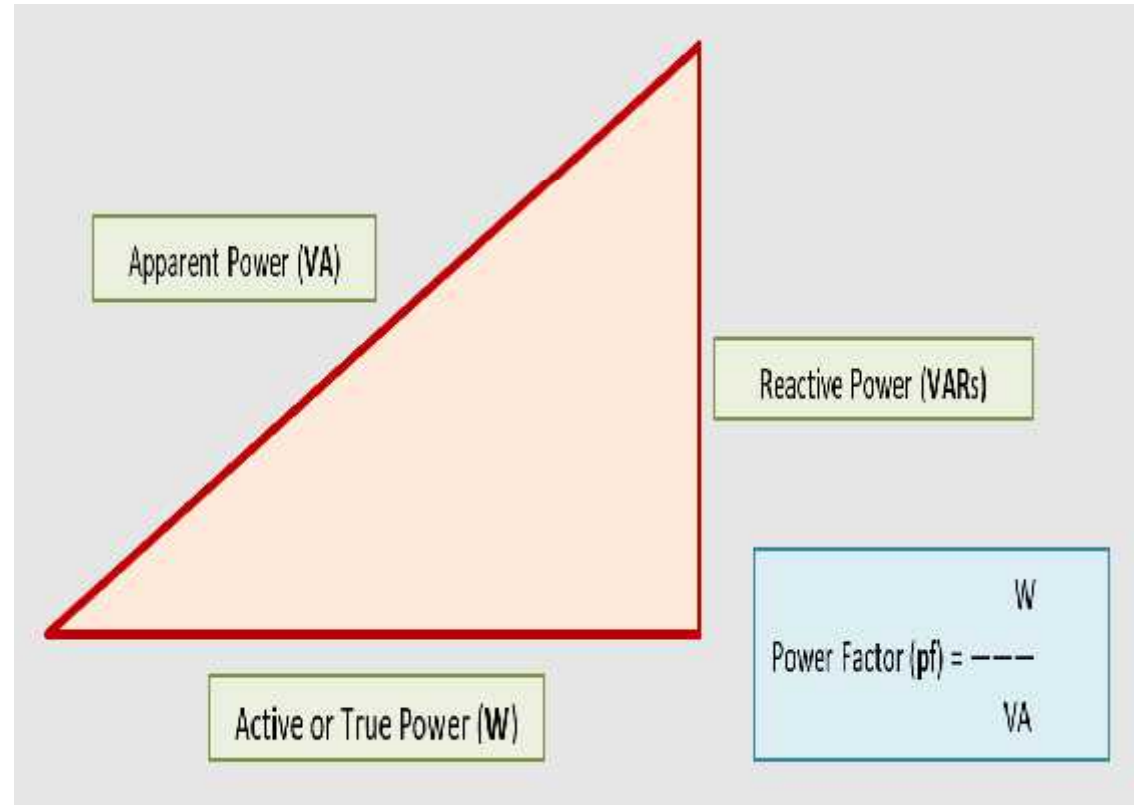


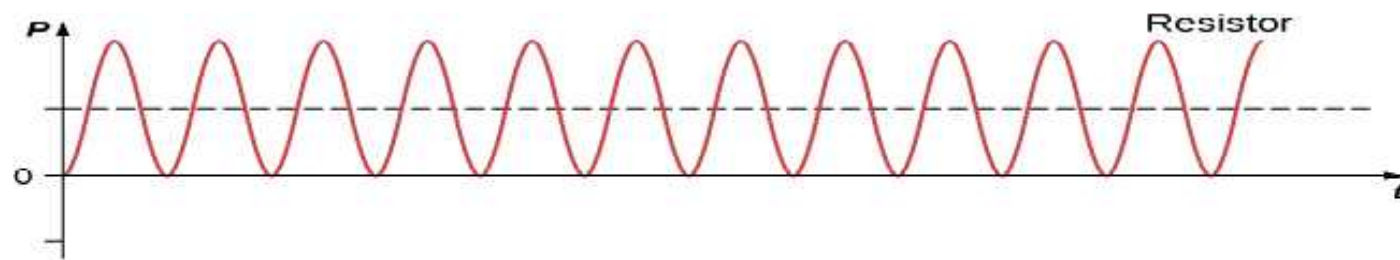


(a)

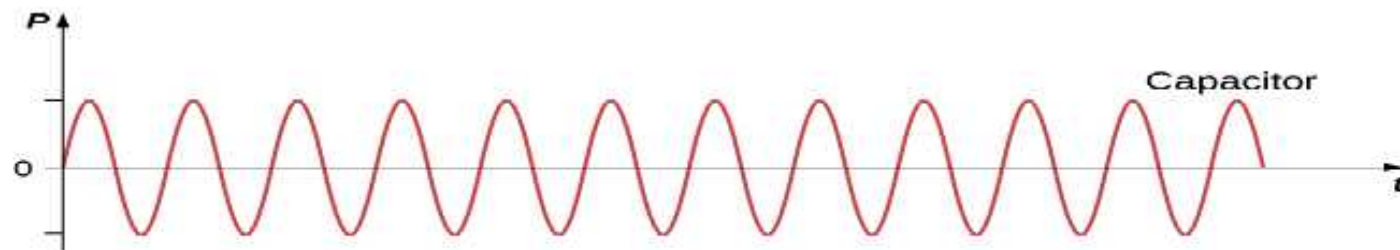

(b)

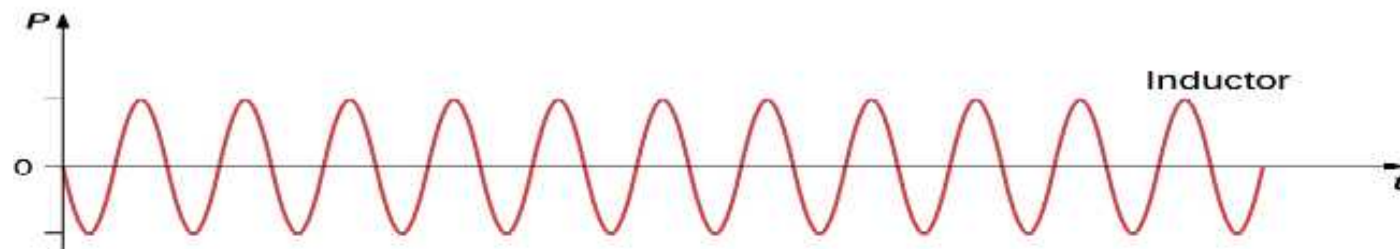

(c)

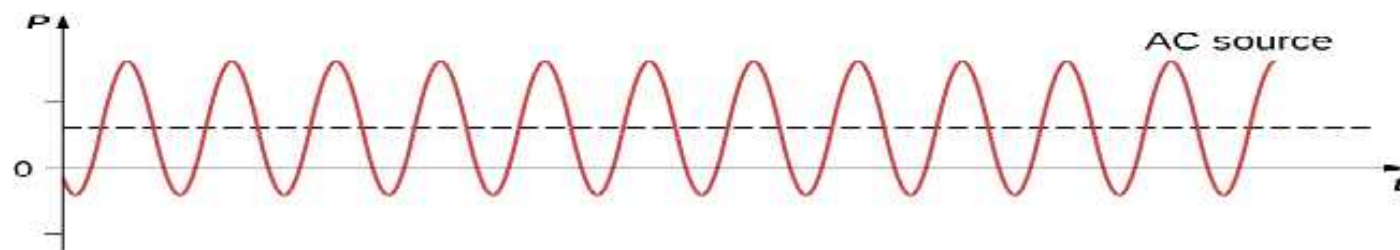

(d)

## Power in AC circuits: Power Factor

$$P = \frac{V_m I_m}{2} \cos \theta \quad (\text{watts, W})$$

- When the load is a combination of resistive and reactive elements, Power factor will vary between 0 and 1
- More resistive the total impedance, the closer the power factor is to 1
- More reactive the total impedance, the closer the power factor is to 0

In terms of the average power and the terminal voltage and current

$$F_p = \cos \theta = \frac{P}{V_{\text{eff}} I_{\text{eff}}}$$

### leading and lagging power factor:

- If the current leads the voltage across a load, the load has a leading PF
- If the current lags the voltage across the load, the load has a lagging PF

*capacitive networks have leading power factors, and inductive networks have lagging power factors.*

$$\text{Power Factor} = \frac{\text{watts}}{\text{volt-amperes}}$$

$$= \frac{P}{S} = \frac{VI \cos \phi}{VI} = \cos \phi$$

$$\text{Power factor} = \frac{P}{S}$$

$$\text{Power factor} = \frac{1.5\text{kW}}{2.308\text{kVA}}$$

$$\text{Power factor} = 0.65$$

The average **ac power** is found by multiplying the **rms** values of current and **voltage**. Ohm's law for the **rms ac** is found by dividing the **rms voltage** by the impedance. In an **ac circuit**, there is a phase angle between the source **voltage** and the current, which can be found by dividing the resistance by the impedance.


**RMS** value is equal to the **value** of the direct current that would produce the same average power dissipation in a resistive load.

**RMS value of AC** = 0.707 times its instantaneous **value**

Then the **RMS** voltage ( $V_{\text{RMS}}$ ) of a sinusoidal waveform is determined by multiplying the peak voltage value by 0.7071, which is the same as one divided by the square root of two (  $1/\sqrt{2}$  ).
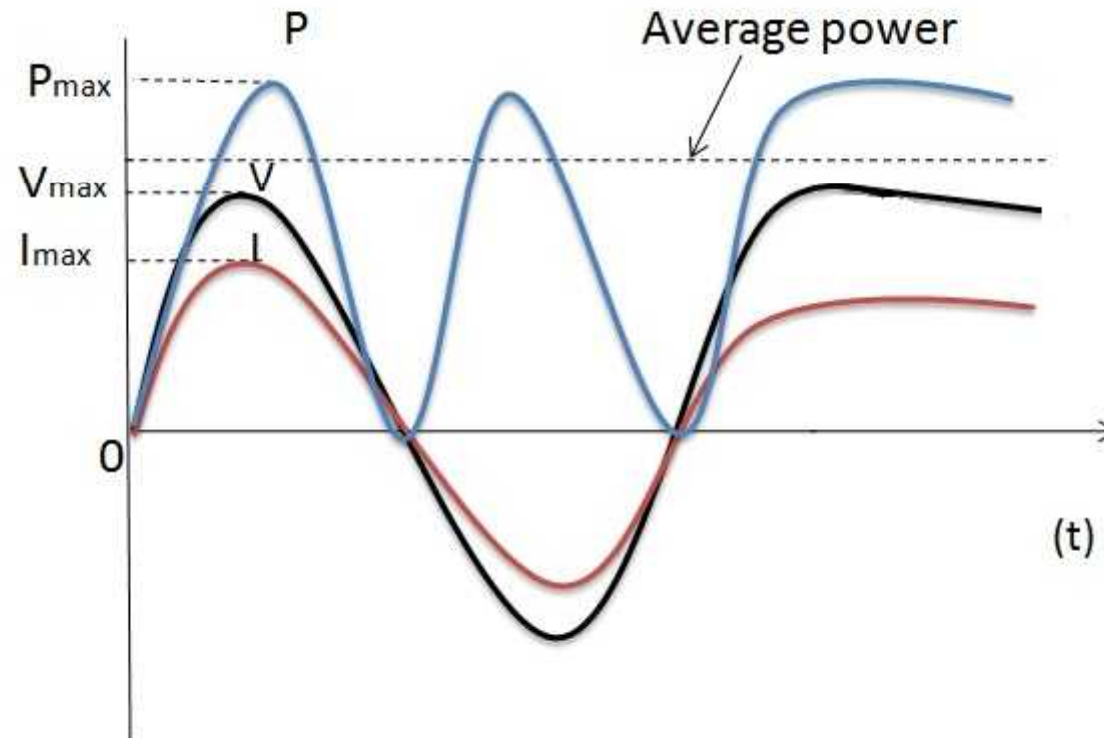
## Power in AC Circuits

Electrical **power** is the “rate” at which **energy** is being consumed in a **circuit** and as such all electrical and electronic components and devices have a limit to the amount of electrical **power** that they can safely handle. For example, a 1/4 watt resistor or a 20 watt amplifier.




# WHAT IS RMS VOLTAGE AND CURRENT?

## WHY DO WE USE RMS VALUES?

Waveform	RMS
DC $y = A_0$	$A_0$
Sine wave $y = A_1 \sin(xt)$	$\frac{A_1}{\sqrt{2}}$
Square wave $y = A_1 \quad 0 < t < 0.5T$ $y = -A_1 \quad 0.5T < t < T$	$A_1$
Triangle Sawtooth	$\frac{A_1}{\sqrt{3}}$
DC shifted sine wave $y = A_0 + A_1 \sin(xt)$	$\sqrt{A_0^2 + \frac{A_1^2}{2}}$
DC shifted square wave $y = A_1 + A_0 \quad 0 < t < 0.5T$ $y = -A_1 + A_0 \quad 0.5T < t < T$	$\sqrt{A_0^2 + A_1^2}$
Sine wave + Square wave $y = A_0 + A_1 \sin(xt) \quad 0 < t < 0.5T$ $y = -A_0 + A_1 \sin(xt) \quad 0.5T < t < T$	$\sqrt{A_0^2 + \frac{A_1^2}{2}}$
Pulse train $y = 0 \quad 0 < t < t_1$ $y = A_1 \quad t_1 < t < T$	$A_1 \sqrt{\frac{T - t_1}{T}}$

$$RMS_{wave} = \sqrt{\frac{\sum_{i=1}^n v_i^2}{n}} = \sqrt{\frac{v_1^2 + v_2^2 + \dots + v_n^2}{n}}$$
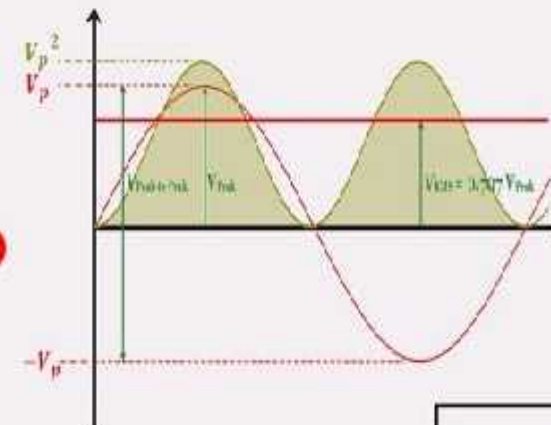
$$v_{RMS} = \sqrt{\frac{1}{T_2 - T_1} \int_{T_1}^{T_2} (V_p \sin(\omega t))^2 dt}$$



120 Volts<sub>RMS</sub> = 340 Volts<sub>pp</sub>

$$RMS \text{ Value}_{\text{sine wave}} = \frac{v_{peak}}{\sqrt{2}} = 0.707 v_{peak}$$

